

## Assignment-3 (Y22)

Implement the following circuits in Verilog:

### 1. Four-Bit-Binary Counter

Problem Statement: Build a 4-bit binary counter that counts from 0 through 15, inclusive, with a period of 16. The reset input is synchronous, and should reset the counter to 0.

### 2. Four-Bit- Decimal Counter

Problem Statement : Build a 4-digit BCD (binary-coded decimal) counter. Each decimal digit is encoded using 4 bits: q[3:0] is the ones digit, q[7:4] is the tens digit, etc. For digits [3:1], also output an enable signal indicating when each of the upper three digits should be incremented.

### 3. Left/Right Rotator

Problem Statement: Build a 100-bit left/right rotator, with synchronous load and left/right enable. A rotator shifts-in the shifted-out bit from the other end of the register, unlike a shifter that discards the shifted-out bit and shifts in a zero. If enabled, a rotator rotates the bits around and does not modify/discard them.

- load: Loads shift register with data [ 99 : 0 ] instead of rotating.
- ena [ 1 : 0 ]: Chooses whether and which direction to rotate.
  - 2 ' b01 rotates right by one bit
  - 2 ' b10 rotates left by one bit
  - 2 ' b00 and 2 ' b11 do not rotate.
- q: The contents of the rotator.

☐ Finite State Machines


Watch the below 2 lectures on Verilog modeling of Finite State Machines and attempt the following example for better understanding and practice.

<https://youtu.be/Ln7dAZtRnFY?si=g4jcrJFLP7vWla2F>

<https://youtu.be/mEm4I5wNm1A?si=W80--E2XKNCWq1pq>

Write a Verilog code to design Moore State Machine:

 Moore state machine with two states, one input, and one output. Implement this state machine. Notice that the reset state is B.



```
1) module four_bit_binary_counter(  
    input clk,  
    input reset,  
    output reg[3:0] z  
);  
always @(posedge clk or posedge reset) begin  
    if (reset) begin  
        z <= 4'b0000;  
    end  
    else begin  
        if (z == 4'b1111) begin  
            z <= 4'b0000;  
        end  
        else begin  
            z <= z + 1;  
        end  
    end  
end  
endmodule
```

Roll.No.220280

```

2) module bcd_counter(
    input clk,
    input reset,
    output reg [15:0] q,
    output reg en1,
    output reg en2,
    output reg en3
);

    always@(posedge clk or posedge reset) begin
        en1<=0; en2<=0; en3=0;
        if(reset) q<=16'd0;

        if(q[3:0] == 4'd9) begin
            q[3:0] <= 4'd0;
            en1 <= 1;

            if(q[7:4] == 4'd9) begin
                q[7:4] <= 4'd0;
                en2 <= 1;

                if(q[11:8] == 4'd9) begin
                    q[11:8] <= 4'd0;
                    en3 <=1;
                    q[15:12] = q[15:12] + 1;
                end

                else q[11:8] = q[11:8] + 1;
            end

            else q[7:4] = q[7:4] + 1;
        end

        else q[3:0] = q[3:0] + 1;
    end

endmodule

```

```

3) module rotator (clk,reset,data,load,enable,q);
  input clk,reset,load;
  input [99:0] data;
  input [1:0] enable;
  output reg [99:0] q;

  initial begin q<=100'd0;
  end

  always@(posedge clk or posedge reset) begin
    if(reset) q<=100'd0;
    else if(load) q<=data;
    else begin
      case(enable)
        2'b01 : q<={q[0],q[99:1]};
        2'b10 : q<={q[98:0],q[99]};
        default : q<=q; endcase
      end
    end
  endmodule

```

```

4) module moore (
  input clk,
  input x,
  output reg z,
  output reg ab
);
  parameter A=0,B=1;
  always @(posedge clk)
    case (ab)
      B: begin
        z <= x ? 1 : 0;
        ab <= x ? B : A;
      end
      A: begin
        z <= x ? 1 : 0;
        ab <= x ? A : B;
      end
      default: ab <= B;
    endcase
endmodule

```